

# Laboratory report

Central Application Laboratory

C.A.B. - Elcoma

Eindhoven - the Netherlands

No : ETT 8604

Title : Example for the application  
of the TEA1060 speech circuit  
for the German market

*copy: chBurt*

Author(s) : P. Sijbers

Date : 05-02-1986

Nederlandse Philips Bedrijven N.P.B. Eindhoven - Nederland



Electronic  
components  
and materials

**PHILIPS**





## laboratory report

central application laboratory CAB  
eindhoven - the netherlands

number : ETT8604

date : 1986-02-05

project : AP3202

pages: S1; R16;

title Example for the application of the TEA1060 speech circuit  
for the German market

author P.J.M. Sijbers

### SUMMARY

The German Post Office nowadays requires a complex impedance for telephone sets.

In practice this requirement makes it necessary to rebalance the anti side tone circuit of the TEA1060.

This report gives an example how to rebalance the anti side tone circuit.

Furthermore an application proposal for the TEA1060 is presented, that fulfils the transmission requirements for: Reference equivalents (EBD, SBD, RBD), electrical frequency characteristics, noise, BRL and DC resistance.

P.J.M. Sijbers

Appr. v.d. Kam

The contents of this report are not to be reproduced, in whole or in part, nor disclosed to third parties without the written consent of:  
N.V. Philips' Gloeilampenfabrieken - Eindhoven - The Netherlands  
Product Division Electronic Components and Materials

8222 031 76341

PHILIPS

The contents of this report are not to be reproduced, in whole or in part, nor disclosed to third parties without the written consent of:  
N.V. Philips' Gloeilampenfabrieken - Eindhoven - The Netherlands  
Product Division Electronic Components and Materials

Electronic  
components  
and materials

## I. INTRODUCTION

Beginning 1984 the existing C.A.B. speech/pulse dialling p.c. board nr. 3132 was handed over to German setmakers in order to get feedback from the market. The p.c. board was not intended to present an optimum solution for the German market. A first impression of the performance of this p.c. board has been presented in Ref. 1.

Two problems were encountered:

- the anti side tone circuit of the TEA1060/1061 had to be investigated with complex line matching impedance.
- The DC requirement at 2mA line current was not fulfilled.

In the mean time the anti-side tone circuit of the TEA1060/1061 has been investigated with complex line matching impedance.

The results are described in Ref. 2.

Two possibilities are given in Ref. 2 to rebalance the bridge.

Furthermore it is shown that a changeover to the Wheatstone bridge structure is an alternative.

In order to give somewhat more application support, a proposal for the German market has been worked out, that fulfils the requirements for:

- "Rückflusssdämpfung" (Balance Return Loss) with complex reference impedance
- the electrical frequency characteristics
- the side tone (RBD)
- the send and receive reference equivalents (SRE, RRE)
- noise
- DC resistance of the set.

## II. SOME CONSIDERATIONS

The frequency characteristic of the sending channel loaded with 600  $\Omega$  at the a/b terminals must be nearly flat.

The set impedance must be complex in order to meet the BRL requirement.

Central application laboratory CAB Eindhoven - The Netherlands



Information presented in this report is based on pilot studies in our laboratories. It is presented in good faith but N.V. Philips' Gloeilampenfabrieken assumes no liability for any consequences of its use. Its presentation does not imply a licence under any patent, trademark or copyright.



Because these two requirements are contradictory a compromise has been chosen between BRL and the electrical frequency characteristic by choosing a set impedance of  $825\Omega//33nF$ .

In Appendix I it is shown how to rebalance the anti side tone circuit with this set impedance assuming that a line length of 5km 0,5mm diameter copper twisted pair must give optimum side tone performance.

The circuit diagram is given in Fig. 1.

Note that the dialling part is not designed especially for Germany.

Some tests have been done on the circuit according to the FTZ requirements described in "Übertragungstechnische Bedingungen für Fernsprechapparate FTZ 121R8 (March 1983)"

The latest FTZ ideas about "Schnittstellen" between the transducers and the speech circuit have been taken into account.

### III. RESULTS OF MEASUREMENTS

The number of the following items correspond with the numbers used in FTZ paper: FTZ121R8 (March 1983).

#### 3. "Bezugsdämpfungen"

The "Sendebezugsdämpfung (SBD)"; the "Empfangsbezugsdämpfung (EBD)" and the "Rückhörbezugsdämpfung (RBD)" have been measured on the OBDM measurement set up.

Standard Piezo transducers have been used.

Results:	Measured (dB)	Requirement (dB)
SBD	+0.4	0
EBD	-5.6	-6
1)RBD	14.3	$\geq 10$

1) Weighted total mean value (35 connections)

Not corrected for  $\Delta$  SBD and  $\Delta$  EBD

Table I shows the results for all 35 connections.

Central application laboratory CAB Eindhoven - The Netherlands



PHILIPS

6. FREQUENCY CHARACTERISTICS OF THE AMPLIFIERS6.1 Frequency characteristic sending

Fig. 2 shows the electrical frequency characteristic measured between microphone inputs and the a/b terminals with 600  $\Omega$  load.

$$\left. \begin{array}{l} A_m = 43.6\text{dB at } 300\text{Hz} \\ A_m = 43.7\text{dB at } 1\text{kHz} \\ A_m = 43.3\text{dB at } 3.4\text{kHz} \end{array} \right\} \Delta = -0.4\text{dB}$$

6.3 Frequency characteristic receiving

Fig. 3. shows the electrical frequency characteristic measured between the a/b terminals and the receiver output (loaded with 200 $\Omega$  asymmetrically)

$$\left. \begin{array}{l} A_{TA} = -2.2\text{dB at } 300 \text{ Hz} \\ A_{TA} = -2.2\text{dB at } 1 \text{ kHz} \\ A_{TA} = -1.6\text{dB at } 3.4 \text{ kHz} \end{array} \right\} \Delta = -0.6\text{dB}$$

Note that the complex set impedance causes some extra frequency dependency ( $\approx 0.4\text{dB}$  from 300Hz to 3.4Hz if it is measured with a sine wave generator with 600 $\Omega$  source impedance connected to the a/b terminals.

The contents of this report are not to be reproduced, in whole or in part, nor disclosed to third parties without the written consent of: N.V. Philips' Gloeilampenfabrieken - Eindhoven - The Netherlands Product Division Electronic Components and Materials

Electronic components and materials



Central application laboratory CAB Eindhoven - The Netherlands

Information presented in this report is based on pilot studies in our laboratories. It is presented in good faith but N.V. Philips' Gloeilampenfabrieken assumes no liability for any consequences of its use. Its presentation does not imply a licence under any patent, trademark or copyright.

# PHILIPS

The contents of this report are not to be reproduced, in whole or in part, nor disclosed to third parties without the written consent of:  
N.V. Philips' Gloeilampenfabrieken - Eindhoven - The Netherlands  
Product Division Electronic Components and Materials

Electronic  
components  
and materials



## 9. "Geräuschspannung"

The noise has been measured psophometrically weighted in accordance with CCITT recommendation P53.

$I_{line} = 25\text{mA}$  (corresponding with  $R_V = 1200\Omega$ )

	noise voltage ( $\mu\text{V}$ )	
	measured	Requirement
- a/b line with 600 $\Omega$ load	78	$\leq 200$
- earpiece output with 200 $\Omega$ load	70	$\leq 100$

## 15. "Rückflusdämpfung" (Balance Return Loss)

The balance return loss measured against the required complex reference impedance ( $220\Omega + 820\Omega//115\text{nF}$ ) is shown in Fig. 4.

The FTZ requirement is met.

Central application laboratory CAB Eindhoven - The Netherlands

Information presented in this report is based on pilot studies in our laboratories. It is presented in good faith but N.V. Philips' Gloeilampenfabrieken assumes no liability for any consequences of its use. Its presentation does not imply a licence under any patent, trademark or copyright.



PHILIPS

The contents of this report are not to be reproduced, in whole or in part, nor disclosed to third parties without the written consent of:  
N.V. Philips' Gloeilampenfabrieken - Eindhoven - The Netherlands  
Product Division Electronic Components and Materials

Electronic  
components  
and materials



## 19. "Gleichstrombedingungen"

## Measured results

	Line resistance $R_V(\Omega)$	Requirement $R_{app}(\Omega)$	Measured		
			$I_{line}(mA)$	$V_{line}(V)$	$R_{app}(\Omega)$
Speech condition	$\leq 1530$	$\leq 470$	$\geq 20$		$\leq 320$
	1530	$\leq 470$	20	6,39	320
	27k7	$\leq 2k25$	2	3,96	1k98
	218k	$\leq 22k$	0,25	3,15	12k6
Mute condition	$\leq 1530$	$\leq 325$	$\geq 20$		$\leq 320$

The 2k resistor between pins 1 and 18 of the TEA1060 reduces the voltage drop across the speech circuit at 2mA line current in such a way that the 2k25 requirement can be met.

Requirement for the mosfet used as an interrupter is that:  $R_{dson} \leq 250\Omega$  at  $V_{gs} = 2.0V$ .

The requirement in mute condition is just fulfilled. In order to get somewhat more margin, the voltage drop across the speech circuit can be decreased somewhat by means of a resistor between pins 1 and 16 of the TEA1060. (For details please see Ref. 3).

Central application laboratory CAB Eindhoven - The Netherlands

Information presented in this report is based on pilot studies in our laboratories. It is presented in good faith but N.V. Philips' Gloeilampenfabrieken assumes no liability for any consequences of its use. Its presentation does not imply a licence under any patent, trademark or copyright.

PHILIPS

IV CONCLUSIONS

- FTZ requirements for "Bezugsdämpfungen", electrical frequency characteristics, noise, balance return loss and DC resistance are met.

- An example how to calculate the anti side tone circuit is given assuming that the side tone must be optimized for a certain line impedance (in this case 5km Ø 0,5mm matched with 600Ω).

However in practice the German telephone lines have different diameters (0.4mm and 0.6mm) and they are matched with several impedances. Therefore it is more practical to optimize the side tone empirically (on the OBDM test set up) by juggling components ( $Z_{bal}$  and/or  $R_g$ ). In this way a compromise for all 35 lines can be obtained.

V REFERENCES

1. P.J.M. Sijbers, Some considerations and measurements for the German market on the existing C.A.B. speech/pulse dialling combination. C.A.B. report nr. TTE84107.
2. P.J.M. Sijbers, Description of the anti side tone circuit of the telephone transmission circuits TEA1060/1061. C.A.B. report nr. TTE 84119.
3. P.J.M. Sijbers, Application of the versatile transmission circuits TEA1060 and TEA1061 in full electronic telephone sets. ETT8302.

The contents of this report are not to be reproduced, in whole or in part, nor disclosed to third parties without the written consent of: N.V. Philips' Gloeilampenfabrieken - Eindhoven - The Netherlands Product Division Electronic Components and Materials

Electronic components and materials



Central application laboratory CAB Eindhoven - The Netherlands

Information presented in this report is based on pilot studies in our laboratories. It is presented in good faith but N.V. Philips' Gloeilampenfabrieken assumes no liability for any consequences of its use. Its presentation does not imply a licence under any patent, trademark or copyright.



PHILIPS

The contents of this report are not to be reproduced, in whole or in part, nor disclosed to third parties without the written consent of:  
N.V. Philips' Gloeilampenfabrieken - Eindhoven - The Netherlands  
Product Division Electronic Components and Materials

Electronic  
components  
and materials




## APPENDIX I

### Rebalancing the anti side tone circuit of the TEA1060 with complex set impedance.

Starting points: - a complex set impedance has been chosen  $825\Omega//33\text{nF}$

- optimum side tone suppression must be obtained for a line length of 5km 0,5mm diameter copper twisted pair ( $176\Omega/\text{km}$ ,  $38\text{nF}/\text{km}$ ) matched with  $600\Omega$ .

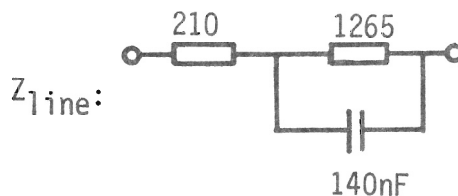The corresponding line impedance can be approximated by




Central application laboratory CAB Eindhoven - The Netherlands

Information presented in this report is based on pilot studies in our laboratories. It is presented in good faith but N.V. Philips' Gloeilampenfabrieken assumes no liability for any consequences of its use. Its presentation does not imply a licence under any patent, trademark or copyright.

PHILIPS

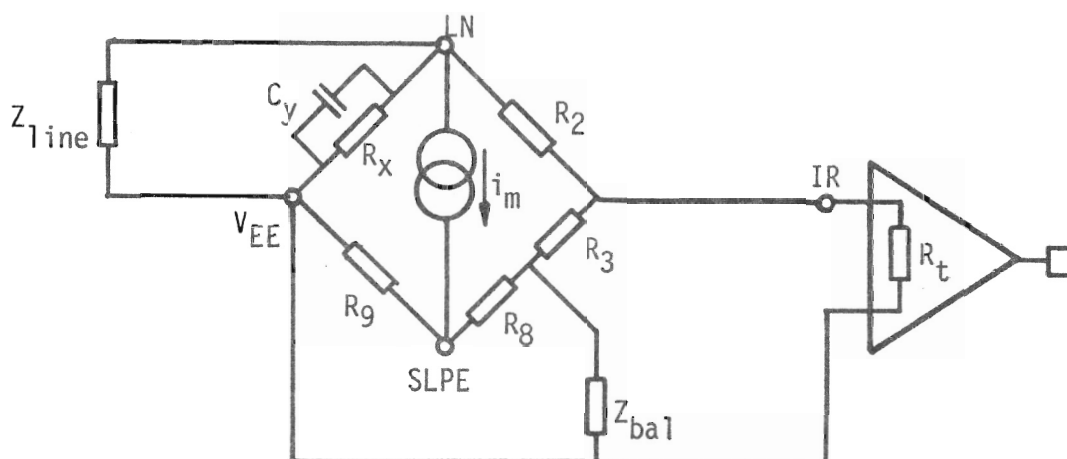Equivalent circuit for the bridge: (Ref. 2)



Original component values with  $R_x = 620\Omega$  and  $CY=0$  and  $Z_{bal}$  optimized for the same  $Z_{line}$  as given above:

$R_2 = 130k$   $R_3 = 3k92$   $R_9 = 20\Omega$   $R_8 = 390\Omega$

$Z_{bal}: 130\Omega + 820\Omega//220nF$

The contents of this report are not to be reproduced, in whole or in part, nor disclosed to third parties without the written consent of: N.V. Philips' Gloeilampenfabrieken - Eindhoven - The Netherlands Product Division Electronic Components and Materials

Electronic components and materials




Central application laboratory CAB Eindhoven - The Netherlands

Information presented in this report is based on pilot studies in our laboratories. It is presented in good faith but N.V. Philips' Gloeilampenfabrieken assumes no liability for any consequences of its use. Its presentation does not imply a licence under any patent, trademark or copyright.



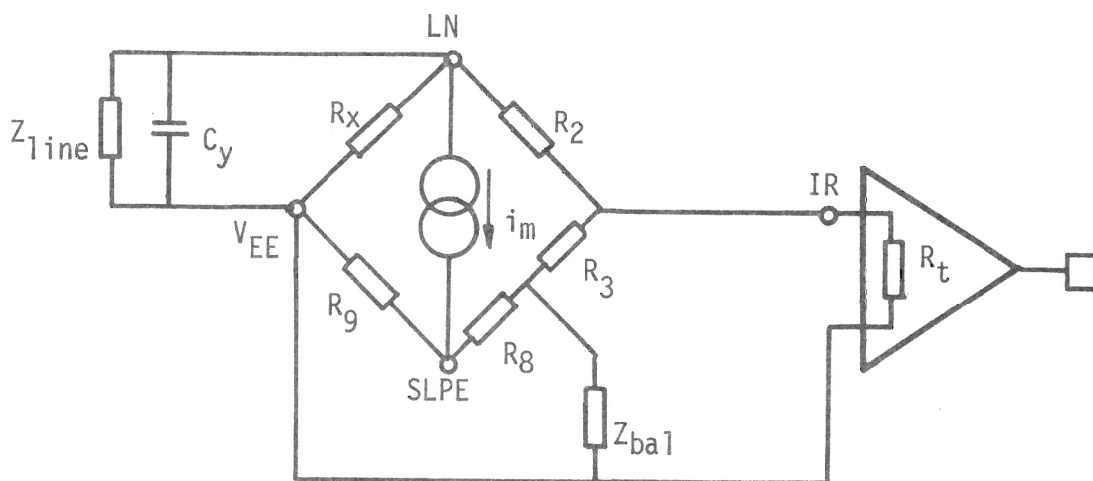Rearranging  $C_Y$  shows that  $C_Y$  can be considered as a part of the line impedance:



From Ref. 2. we know that the bridge is balanced when

$$a. R_9 R_2 = R_X (R_3 + (R_8 // Z_{ba1}))$$

$$b. Z_{ba1} = \frac{R_8}{R_X} (Z_{line} // Z_Y) = k (Z_{line} // Z_Y)$$

$$\text{in this case } Z_Y = \frac{1}{j\omega C_Y}$$

Because  $R_X$  has a larger value ( $825\Omega$ ) than the original  $620\Omega$  ( $R_1$ ) this means that the bridge can be rebalanced by increasing  $R_2$  or by increasing  $R_9$ .

Because Piezo earpieces (which are insensitive) are used in Germany, a large receiving gain will be necessary.

Therefore the bridge attenuation should not be increased by increasing  $R_2$ . The alternative (increasing  $R_9$ ) has been chosen.

Central application laboratory CAB Eindhoven - The Netherlands





$R_g$  originally had a value of  $20\Omega$ .


The new value for  $R_g$  ( $R'_g$ ) can be calculated very simple:

$$R'_g = \frac{R_X}{R_1} R_g = \frac{825}{620} \cdot 20 = 26,6\Omega \text{ (standard value } 27\Omega)$$

Calculating  $Z_{bal}$  and  $R_8$

$Z_{bal}$  must be chosen in accordance with the line impedance in parallel with  $C_Y$ .

$Z_{line} // Z_Y$ :

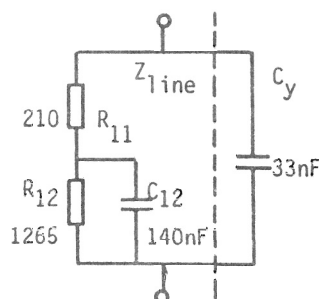


In order to obtain a standard value for the capacitor in  $Z_{line}$  and to fulfil condition a), scale factor  $k$  has been chosen  $k = \frac{140nF}{220nF} = 0,64$ .

This results in:

$$R_8 = k R_X = 0,64 \cdot 825 = 525\Omega$$

$Z_{bal}$ :

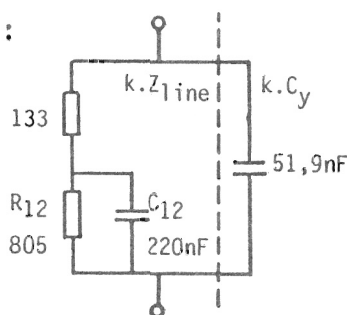

Central application laboratory CAB Eindhoven - The Netherlands



# PHILIPS

Taking standard values for components; the final result

$$\text{is: } R_8 = 510\Omega \quad R_{11} = 130\Omega \quad R_{12} = 820\Omega$$

$$C_{12} = 220\text{nF} \quad kC_Y = 56\text{nF}$$

In this case  $Z_{ba1}$  cannot be simplified, which means that one extra capacitor is needed in  $Z_{ba1}$  to compensate for the influence of  $C_Y$ .

The contents of this report are not to be reproduced, in whole or in part, nor disclosed to third parties without the written consent of:  
N.V. Philips' Gloeilampenfabrieken - Eindhoven - The Netherlands  
Product Division Electronic Components and Materials

Electronic  
components  
and materials



Central application laboratory CAB Eindhoven - The Netherlands

Information presented in this report is based on pilot studies in our laboratories. It is presented in good faith but N.V. Philips' Gloeilampenfabrieken assumes no liability for any consequences of its use. Its presentation does not imply a licence under any patent, trademark or copyright.

Table I Reference Equivalents

measured with  $C_m = 33nF$ 

transducers: Siemens S8 and H8 in handset "71"

Meßverbindung	Gruppennummer	Gewichtung $n$	Meßwert [dB]	$\Sigma$ Meßwert [dB]	$\bar{X}$ Meßwert [dB]	$\bar{X}$ Meßwert gewichtet [dB]	$\Sigma \bar{X}$ Meßwert gewichtet
			$\frac{\text{Max} + \text{Min}}{2}$	Gruppe	$\frac{\text{Gruppe}}{5}$	$\frac{\text{Gruppe}}{5} \cdot n$	
1 2 3 4 5	1	1	10,9 11,3 12,1 9,8 21	65,1	13,02	13,02	299,8 dB
6 7 8 9 10	2	5	8,5 10 10 8,3 17,3	54,1	10,82	54,1	$\frac{\Sigma \bar{X} \text{ Meßwert}}{21}$ (RBD) 14,27 dB
11 12 13 14 15	3	8	13,4 12,7 15,6 11,4 24,5	77,6	15,52	124,16	SBD + 0,4 dB
16 17 18 19 20	4	2	17,3 14,6 21 14,3 20,1	87,3	17,46	34,32	EBD - 5,6 dB
21 22 23 24 25	5	1	17,7 15,6 19,3 15,9 17,3	85,8	17,16	17,16	
26 27 28 29 30	6	2	15,9 10,5 12,6 13 18,3	70,3	14,06	28,12	
31 32 33 34 35	7	2	16,4 12,4 15 13,6 13,4	70,8	14,16	28,32	

i.e. Asymmetrical earpiece connection is assumed.  
Symmetrical earpiece connection is also possible. In that case the corresponding value for  $R_4 = 143k$ .

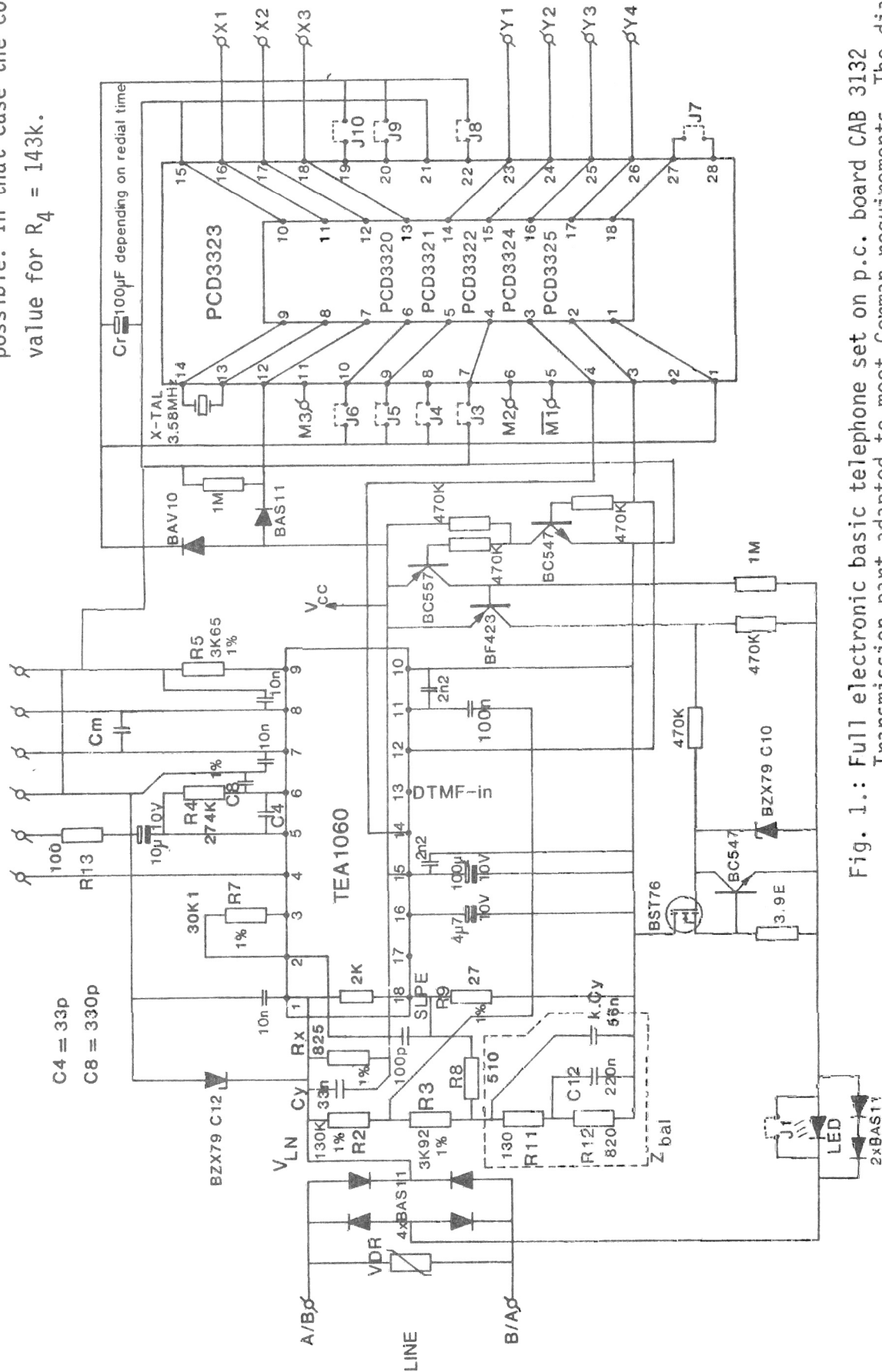


Fig. 1.: Full electronic basic telephone set on p.c. board CAB 3132  
Transmission part adapted to meet German requirements. The dialling part is unchanged. Microphone "Schnittstelle":

FTZ requirement of TEA1060 (pins 7 and 8) is typical 8k6.

Input impedance of TEA1060 (pins 7 and 8) is typical 8k6  
(upper and lower limits are 10k2 and 7k2)  
 $C_m = 47nF - (C_{pin7} + C_{pin8})/2 = 42nF$

# PHILIPS

The contents of this report are not to be reproduced, in whole or in part, nor disclosed to third parties without the written consent of N.V. Philips' Gloeilampenfabrieken - Eindhoven - The Netherlands  
Product Division Electronic Components and Materials

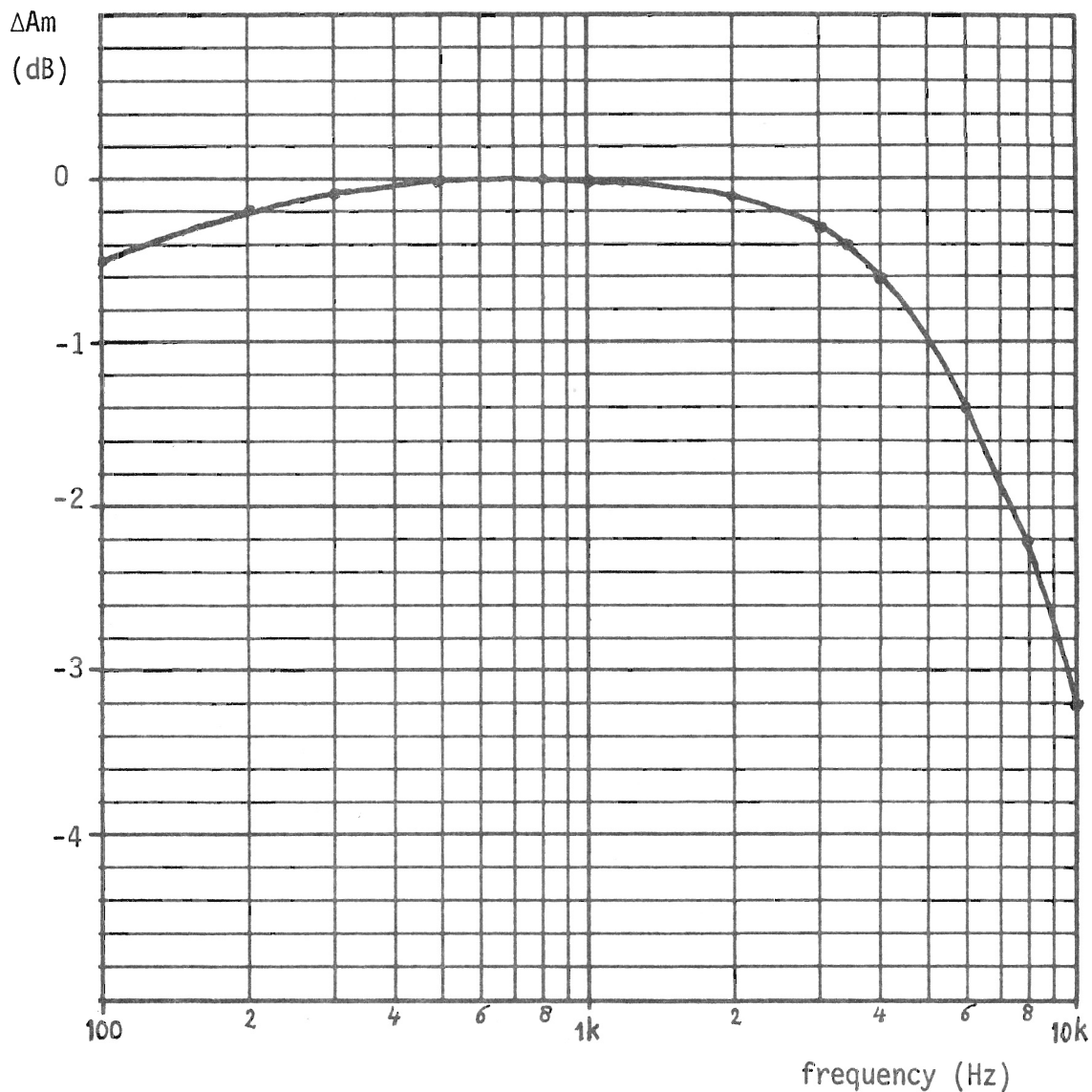


Fig. 2 Electrical frequency characteristic sending  
0dB = 43,7dB gain  
600 $\Omega$  load at a/b

Electronic  
components  
and materials



Central application laboratory CAB Eindhoven - The Netherlands

Information presented in this report is based on pilot studies in our laboratories. It is presented in good faith but N.V. Philips' Gloeilampenfabrieken assumes no liability for any consequences of its use. Its presentation does not imply a licence under any patent, trademark or copyright.



# PHILIPS

The contents of this report are not to be reproduced, in whole or in part, nor disclosed to third parties without the written consent of N.V. Philips' Gloeilampenfabrieken - Eindhoven - The Netherlands Product Division Electronic Components and Materials

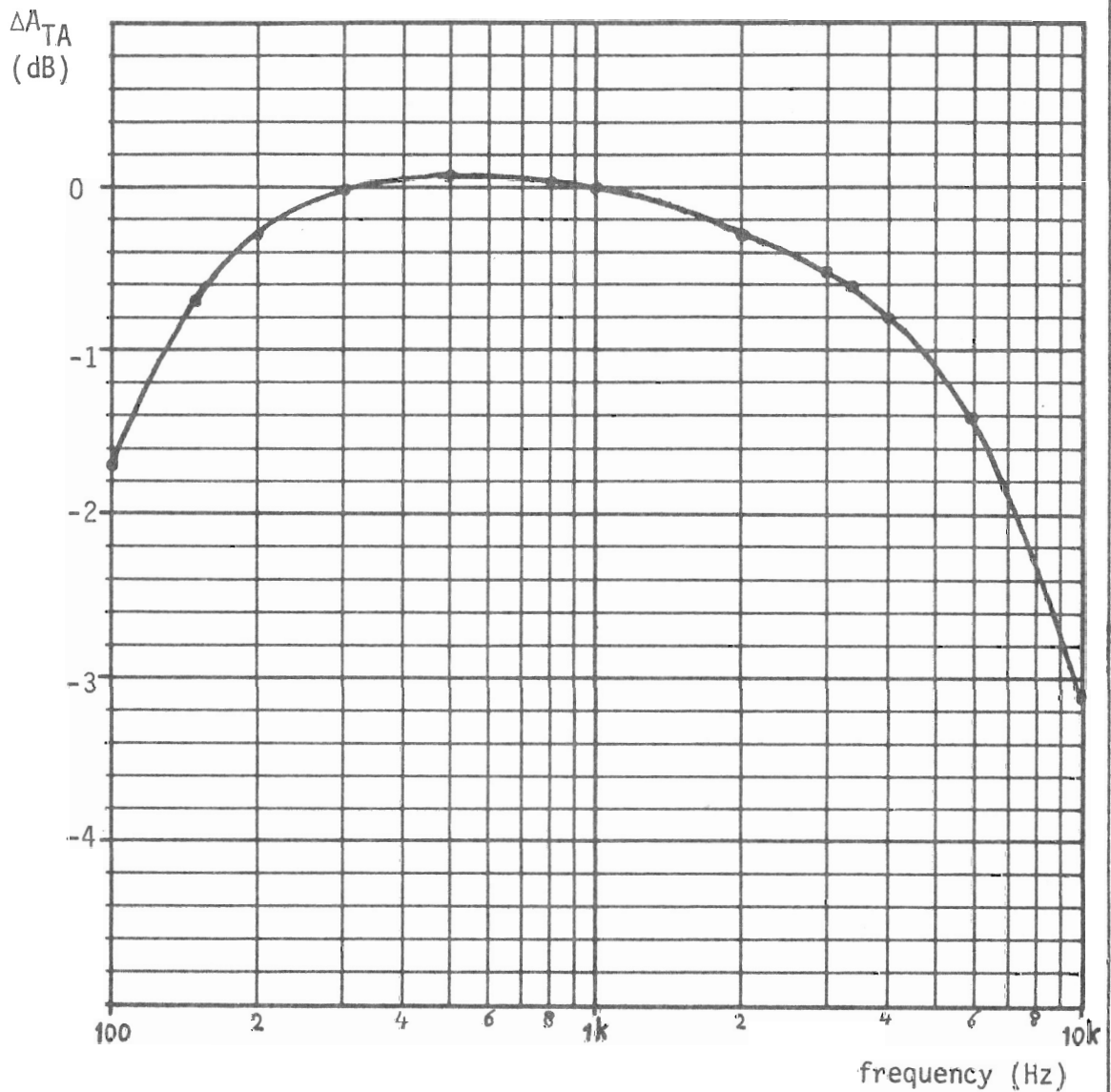


Fig. 3: Electrical frequency characteristic receiving

0dB = -2,2dB gain

200 $\Omega$  load at receiver output.


Measured from a/b to receiver output.

Electronic  
components  
and materials




Central application laboratory CAB Eindhoven - The Netherlands

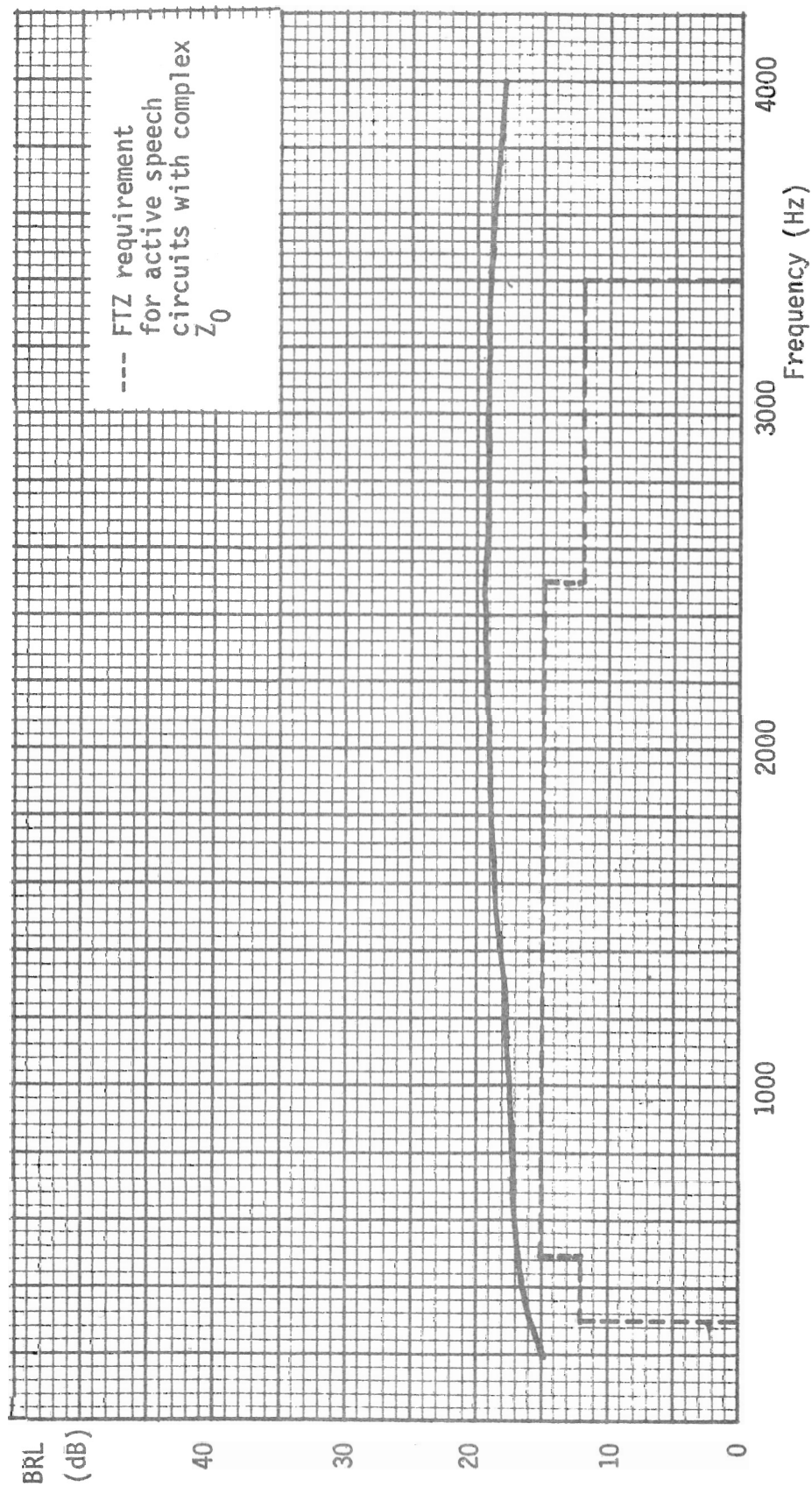Information presented in this report is based on pilot studies in our laboratories. It is presented in good faith but N.V. Philips' Gloeilampenfabrieken assumes no liability for any consequences of its use. Its presentation does not imply a licence under any patent, trademark or copyright.



$$\left| \frac{Z + Z_0}{Z - Z_0} \right|$$

Fig. 4. Balance Return Loss  $\approx 20 \log$

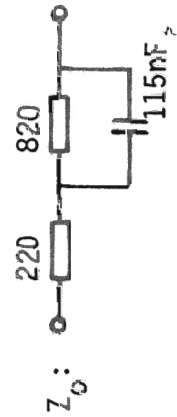

Central application laboratory CAB Eindhoven - The Netherlands



